

Terminal Help

≡ dual_port_ram.v × ≡ tb_dual_port_ram.v

day_087 > project_1 > project_1.srcs > sources_1 > new > ≡ dual_port_ram.v

```

1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Engineer: Anjan Prasad
4  // Create Date: 12/17/2024 10:58:43 AM
5  // Module Name: dual_port_ram
6  ///////////////////////////////////////////////////////////////////
7
8  module dual_port_ram #(
9      parameter DATA_WIDTH = 8,
10     parameter ADDR_WIDTH = 4
11 ) (
12     input clk,
13     input we_a,
14     input we_b,
15     input [ADDR_WIDTH-1:0] addr_a,
16     input [ADDR_WIDTH-1:0] addr_b,
17     input [DATA_WIDTH-1:0] data_a,
18     input [DATA_WIDTH-1:0] data_b,
19     output reg [DATA_WIDTH-1:0] q_a,
20     output reg [DATA_WIDTH-1:0] q_b
21 );
22
23     // Memory declaration
24     reg [DATA_WIDTH-1:0] ram [2**ADDR_WIDTH-1:0];
25
26     // Port A operations
27     always @(posedge clk) begin
28         if (we_a)
29             ram[addr_a] <= data_a;
30         else
31             q_a <= ram[addr_a];
32     end
33
34     // Port B operations
35     always @(posedge clk) begin
36         if (we_b)
37             ram[addr_b] <= data_b;
38         else
39             q_b <= ram[addr_b];
40     end
41
42 endmodule
43

```

Terminal Help

≡ dual_port_ram.v


≡ tb_dual_port_ram.v ×

day_087 > project_1 > project_1.srcs > sim_1 > new > ≡ tb_dual_port_ram.v

```

1  `timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Engineer: Anjan Prasad
4  // Create Date: 12/13/2024 11:02:21 PM
5  // Module Name: tb_dual_port_ram
6  ///////////////////////////////////////////////////////////////////
7
8  module tb_dual_port_ram;
9      parameter DATA_WIDTH = 8;
10     parameter ADDR_WIDTH = 4;
11
12     reg clk;
13     reg we_a, we_b;
14     reg [ADDR_WIDTH-1:0] addr_a, addr_b;
15     reg [DATA_WIDTH-1:0] data_a, data_b;
16     wire [DATA_WIDTH-1:0] q_a, q_b;
17
18     dual_port_ram #(DATA_WIDTH, ADDR_WIDTH) DUT (
19         .clk(clk),
20         .we_a(we_a),      .we_b(we_b),
21         .addr_a(addr_a), .addr_b(addr_b),
22         .data_a(data_a), .data_b(data_b),
23         .q_a(q_a),       .q_b(q_b)
24     );
25
26     initial clk = 0;
27     always #5 clk = ~clk;
28
29     initial begin
30         we_a = 0; we_b = 0;
31         addr_a = 0; addr_b = 0;
32         data_a = 0; data_b = 0;
33
34         // Write to Port A
35         #10 we_a = 1; addr_a = 4'b0010; data_a = 8'hAA;
36         #10 we_a = 0;
37
38         // Write to Port B
39         #10 we_b = 1; addr_b = 4'b0011; data_b = 8'hBB;
40         #10 we_b = 0;
41
42         // Read from Port A
43         #10 addr_a = 4'b0010;
44
45         // Read from Port B
46         #10 addr_b = 4'b0011;
47
48         // Write to both ports simultaneously
49         #10 we_a = 1; we_b = 1;
50         |   addr_a = 4'b0001; data_a = 8'hCC;
51         |   addr_b = 4'b0100; data_b = 8'hDD;
52         #10 we_a = 0; we_b = 0;
53
54         // Read from both ports
55         #10 addr_a = 4'b0001;
56         |   addr_b = 4'b0100;
57
58         #20 $stop;
59     end
60 endmodule

```

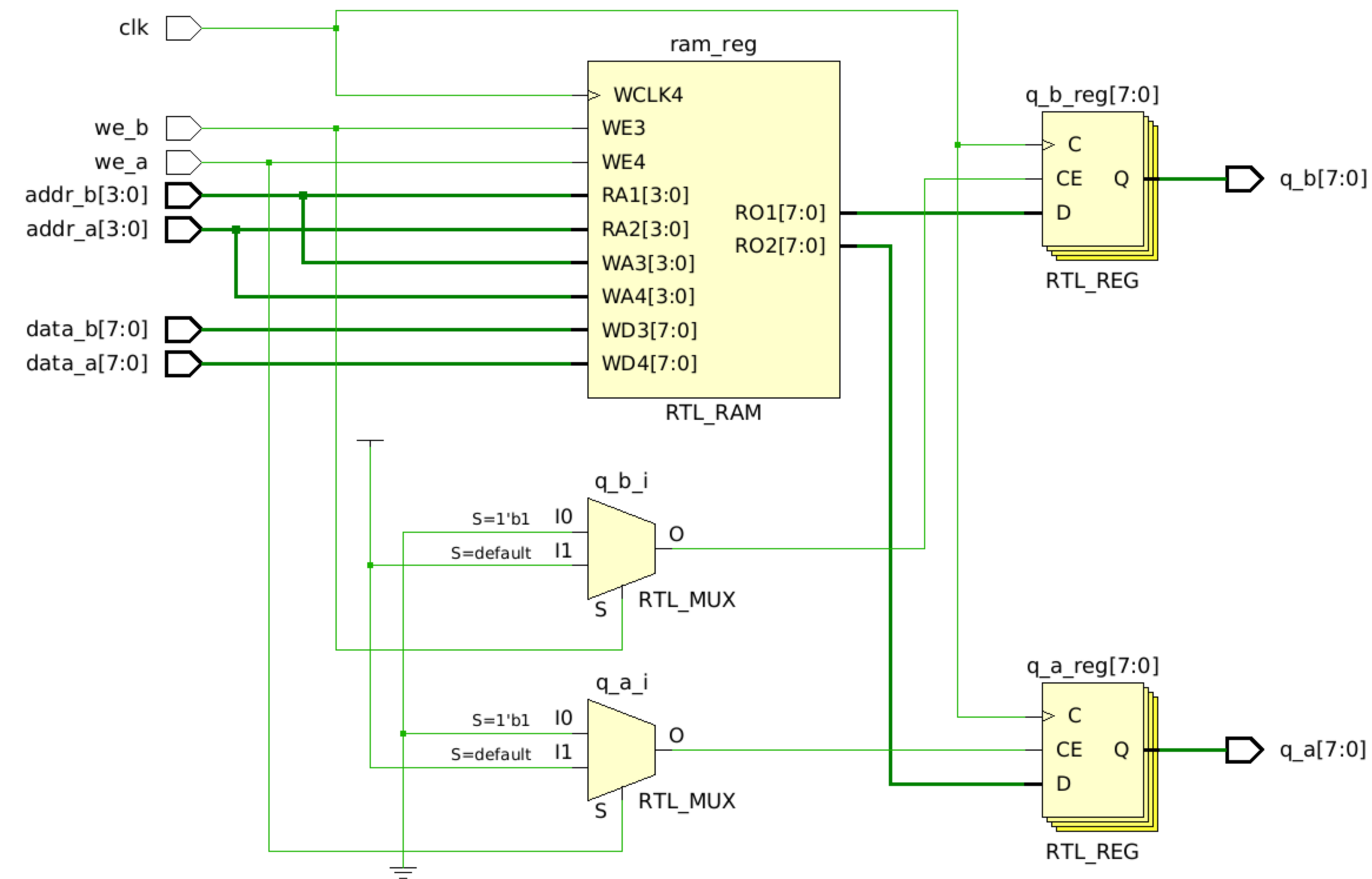




Name

Value

clk	1
we_a	1
we_b	1
> addr_a[3:0]	1
> addr_b[3:0]	4
> data_a[7:0]	204
> data_b[7:0]	221
> q_a[7:0]	170
> q_b[7:0]	187

 

221