










Name	Value
 clk	1
 reset	0
 start	0
 don...	0
>  st...0]	1





  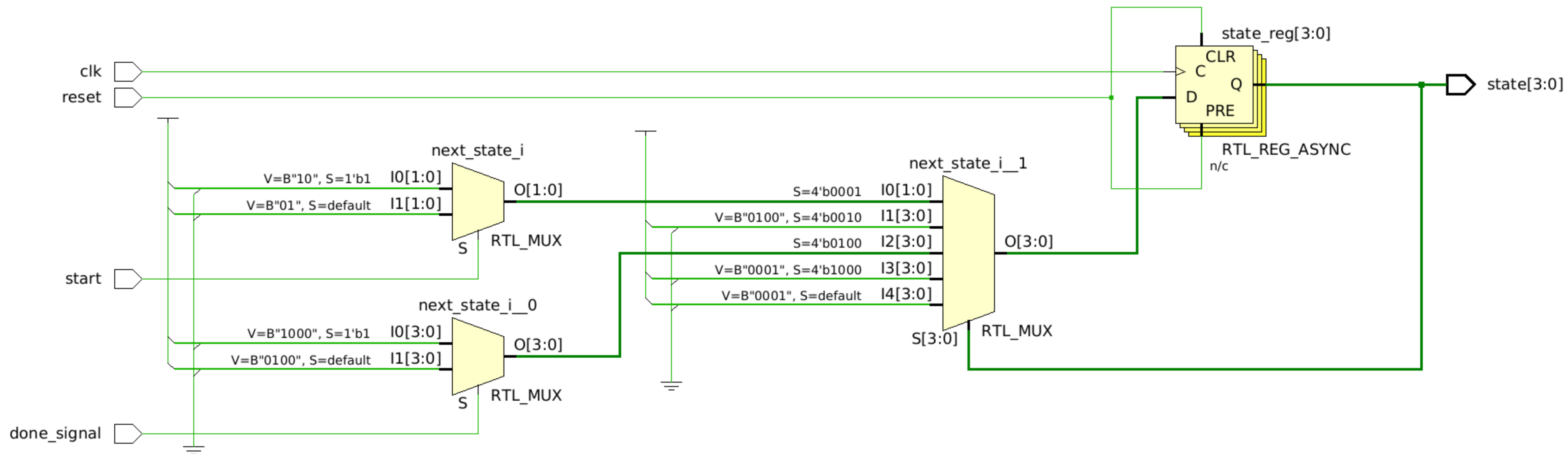

```
1  `timescale 1ns / 1ps
2  //////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
3  // Engineer: Anjan Prasad
4  // Create Date: 12/14/2024 11:28:23 AM
5  // Module Name: fsm_one_hot
6  //////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
7
8  module fsm_one_hot (
9      input clk,reset,start,done_signal,
10     output reg [3:0] state
11 );
12
13     parameter IDLE    = 4'b0001,
14                LOAD    = 4'b0010,
15                PROCESS = 4'b0100,
16                DONE    = 4'b1000;
17
18     reg [3:0] next_state;
19
20     // Sequential Block for State Transition
21     always @(posedge clk or posedge reset) begin
22         if (reset)
23             state <= IDLE;
24         else
25             state <= next_state;
26     end
27     // Combinational Block for Next State Logic
28     always @(*) begin
29         case (state)
30             IDLE:
31                 if (start) next_state = LOAD;
32                 else next_state = IDLE;
33
34             LOAD:
35                 next_state = PROCESS;
36
37             PROCESS:
38                 if (done_signal) next_state = DONE;
39                 else next_state = PROCESS;
40
41             DONE:
42                 next_state = IDLE;
43
44             default:
45                 next_state = IDLE; // Default to IDLE for safety
46         endcase
47     end
48 endmodule
49
50
```



```
1  timescale 1ns / 1ps
2  ///////////////////////////////////////////////////////////////////
3  // Engineer: Anjan Prasad
4  // Create Date: 12/14/2024 11:29:19 AM
5  // Module Name: tb_fsm_one_hot
6  ///////////////////////////////////////////////////////////////////
7
8  module tb_fsm_one_hot;
9
10     reg clk;
11     reg reset;
12     reg start;
13     reg done_signal;
14     wire [3:0] state;
15
16     fsm_one_hot DUT (
17         .clk(clk),
18         .reset(reset),
19         .start(start),
20         .done_signal(done_signal),
21         .state(state)
22     );
23
24     initial begin
25         clk = 0;
26         forever #5 clk = ~clk; // 10ns clock period
27     end
28
29     initial begin
30         reset = 1; start = 0; done_signal = 0; #15;
31
32         reset = 0; #10;
33
34         start = 1; #10;
35
36         start = 0; #20;
37
38         done_signal = 1; #10;
39
40         done_signal = 0; #20;
41
42         $finish;
43     end
44
45     initial begin
46         $monitor("Time = %0t | Reset = %b | Start = %b | Done = %b | State = %b",
47             $time, reset, start, done_signal, state);
48     end
49
50 endmodule
```